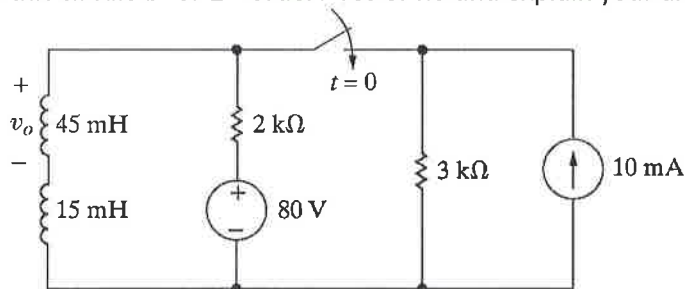



**Short Answer Questions (20 pts)**

1. Circuit Order: Is this circuit 1<sup>st</sup> or 2<sup>nd</sup> order? Yes or no and explain your answer.



1st order - 2 inductors in series can be replaced by  $L_{eq} = L_1 + L_2 = 60 \text{ mH}$

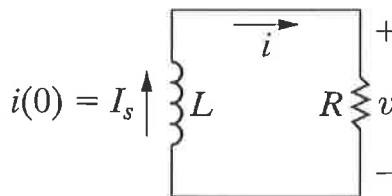2. Time Constants in First-Order Circuits: For the circuit shown below, we showed in class that  $i(t) = I_s e^{-t/\tau}$ , for  $t \geq 0$ . Approximately, how many time constants,  $\tau$ , does it take for the inductor current to be at 2% of the initial current value? Approximately, how many time constants does it take for the resistor to dissipate 98% percent of the initial energy stored in the inductor?



$i(4\tau) \approx 0.02 I_s \Rightarrow$  4 time constants for the inductor current

$w_R(t) = \frac{1}{2} L I_s^2 (1 - e^{-2t/\tau})$

$w_R(2\tau) \approx \frac{1}{2} L I_s^2 (1 - e^{-4}) \approx 0.98 \frac{1}{2} L I_s^2 \Rightarrow$  2 time constants for the energy

3. RLC Damping: In a series RLC circuit, for fixed values of L and C, how does changing the value of R changes the damping of the circuit?

$$\alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$\alpha > \omega_0$  - overdamped

$\alpha < \omega_0$  - underdamped

$\alpha = \omega_0$  - critically damped

$$R = R_{crit} = 2\sqrt{\frac{L}{C}}$$

critical damping

$$\frac{R_{crit}}{2L} = \frac{1}{\sqrt{LC}} \Rightarrow R_{critical} = 2\sqrt{\frac{L}{C}}$$


$\Rightarrow R > 2\sqrt{\frac{L}{C}}$  - overdamped

$R < 2\sqrt{\frac{L}{C}}$  underdamped

4. Continuity of the Capacitor Voltage: Give a short explanation of why the voltage across a capacitor cannot change instantaneously or equivalently it is continuous.

$$v_c(t_0^-) = v_c(t_0^+)$$

If  $v_c(t_0^-) \neq v_c(t_0^+)$  then

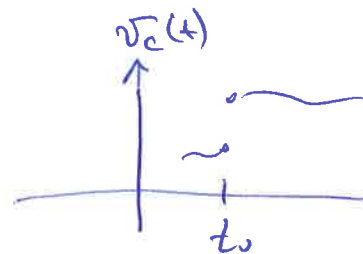


that will imply that  $\frac{dv_c}{dt}(t_0) = \infty$

Note that



$$w_c = \frac{1}{2} C v_c^2 \Rightarrow p_c = C v_c \frac{dv_c}{dt}$$

If  $\frac{dv_c}{dt} = \infty \rightarrow p_c = \infty \Rightarrow$  infinite power is not physically possible.

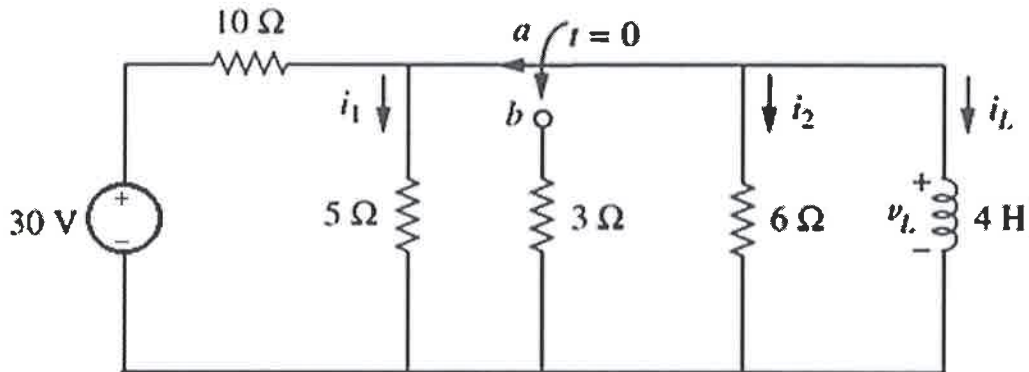
5. For the circuit shown below, the switch is in position **a** for a long time before changing to position **b** at  $t=0$ . (40 points)



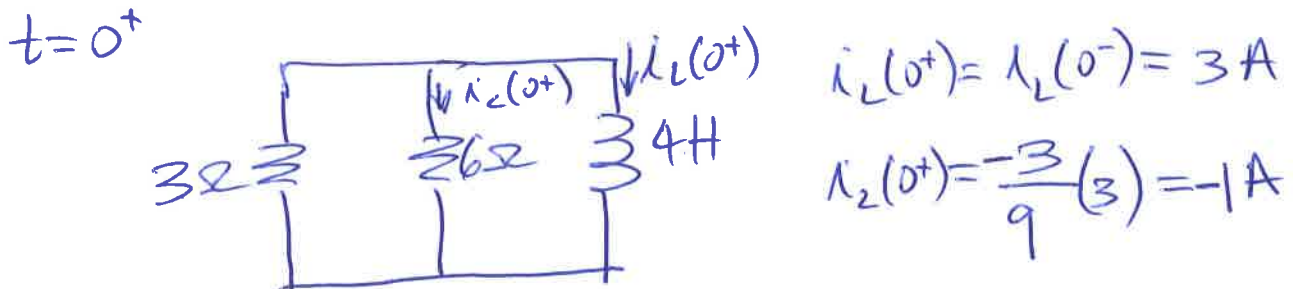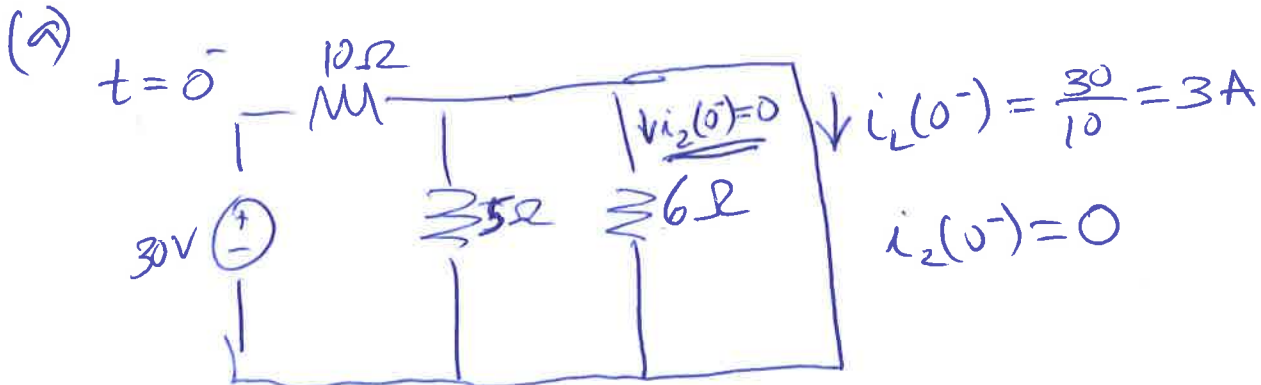- Find  $i_2(0^-)$  and  $i_2(0^+)$ .
- Is  $i_2(0^-) = i_2(0^+)$ ? Answer yes or no and explain your answer.
- Determine the time constant of the circuit for  $t > 0$ .
- Write the expression for  $i_L(t)$  for  $t \geq 0$ .
- Find the energy stored in the 4H inductor at  $t=0$ .
- What percentage of the initial energy stored in the inductor is dissipated in the 6Ω resistor?



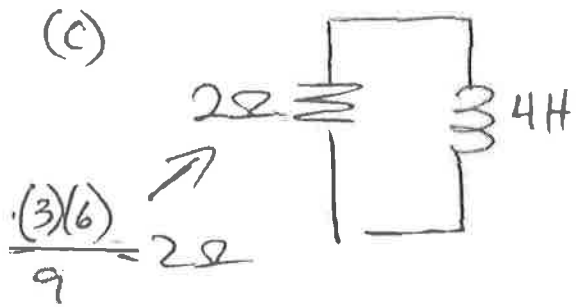(b)  $\Rightarrow i_2(0^-) \neq i_2(0^+) \rightarrow$  current through a resistor is not continuous.



$$\tau = \frac{L}{R} = \frac{4}{2} = 2 \text{ sec}$$

$$(d) i_L(t) = I_0 e^{-t/\tau}, t \geq 0$$

$$i_L(t) = 3 e^{-t/2}, t \geq 0$$

$$(e) w_L(0) = \frac{1}{2} L i_L^2(0) = \frac{1}{2} 4 (3)^2 = 18 \text{ J}$$


$$(f) i_2(t) = -\frac{3}{9} i_L(t) = -\frac{1}{3} (3e^{-t/2}) = -e^{-t/2}, t \geq 0$$

$$P_{6\Omega}(t) = i_2^2 R = 6 e^{-t}, t \geq 0$$


$$W_{6\Omega} = \int_0^{\infty} 6 e^{-t} dt = -6 e^{-t} \Big|_0^{\infty} = 6 \text{ J}$$

$$\% = \frac{W_{6\Omega}}{w_L(0)} = \frac{6}{18} = \frac{1}{3} \Rightarrow 33\% \text{ of the total energy is dissipated in the } 6\Omega \text{ resistor.}$$

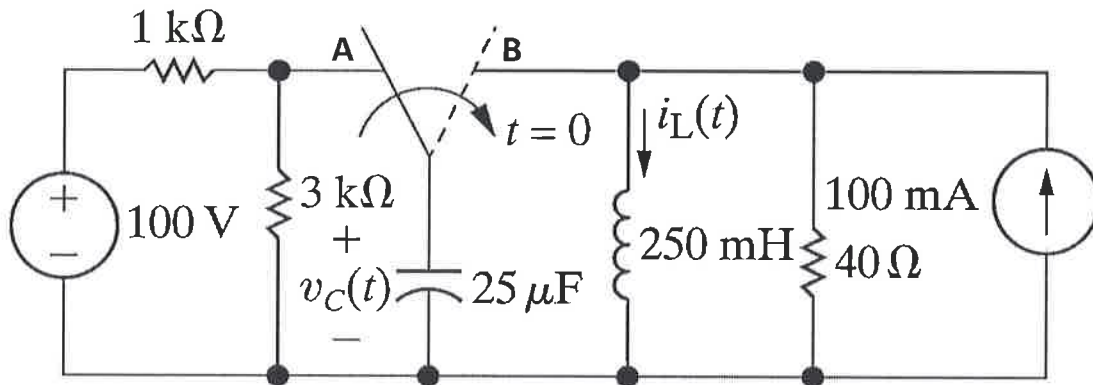6. For the circuit shown below, the switch has been in position A for a long time before switching to position B at  $t=0$  (40 points).




- Draw a sketch of the state of the circuit just before the switch changes to position B (e.g.  $t=0^-$ ). Find  $i_L(0^-)$  and  $v_c(0^-)$ .
- Draw a sketch of the state of the circuit just after the switch changes to position B (e.g.  $t=0^+$ ). Find  $i_L(0^+)$  and  $v_c(0^+)$ .
- Draw a sketch of the state of the circuit after the switch has been in position B for a long time ( $t \rightarrow \infty$ ). Find  $i_L(\infty)$  and  $v_c(\infty)$ .
- Calculate the resonant radian,  $\omega_o$ , and the neper frequency,  $\alpha$ , for the circuit.
- Determine if the transient response of the circuit is overdamped, critically damped, or underdamped.
- Write the expression for the inductor current,  $i_L(t)$  for  $t \geq 0$ .

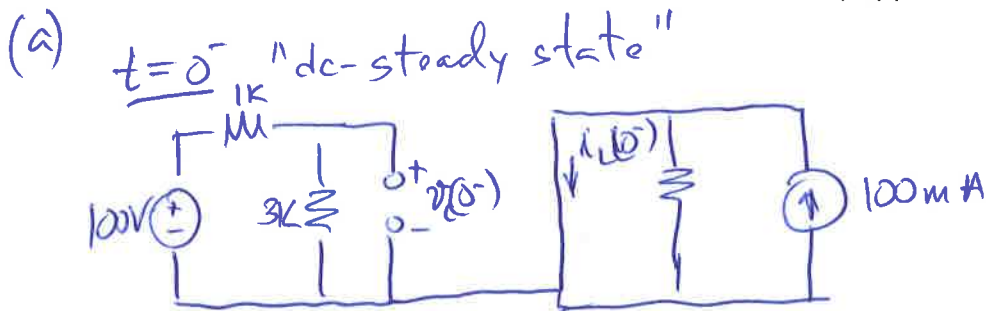


$$v_c(0^-) = \frac{3}{4}(100) = 75V$$

$$i_L(0^-) = 100mA = 0.1A$$

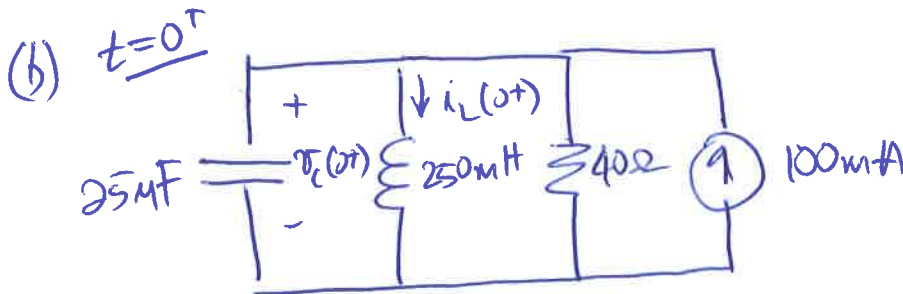

$$v_c(0^+) = v_c(0^-) = 75V$$

$$i_L(0^+) = i_L(0^-) = 100mA = 0.1A$$

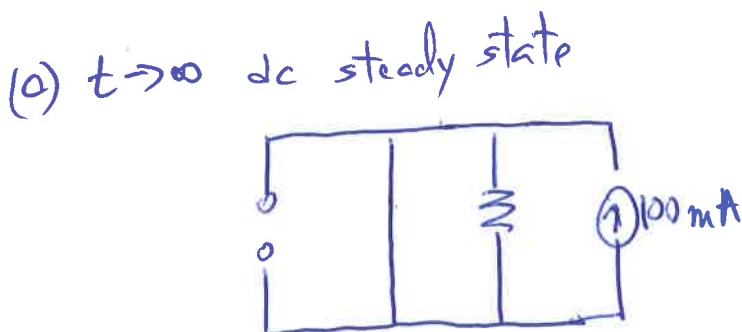

$$v_c(\infty) = 0$$

$$i_L(\infty) = 100mA = 0.1A$$

$$(d) \alpha = \frac{1}{2RC} = \frac{1}{2(40)(25 \times 10^{-6})} = 500 \text{ rad/sec.}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(250 \times 10^{-3})(25 \times 10^{-6})}} = \frac{10^4}{25} = 400 \text{ rad/sec}$$

(e)  $\alpha > \omega_0 \Rightarrow$  overdamped

$$(f) i_L(t) = I_f + A_1 e^{+s_1 t} + A_2 e^{+s_2 t}, \quad t > 0$$

$$\begin{aligned} s_{1,2} &= -500 \pm \sqrt{(500)^2 - (400)^2} \\ &= -500 \pm \sqrt{25 \times 10^4 - 16 \times 10^4} = -500 \pm \sqrt{9 \times 10^4} \\ &= -500 \pm 300 \end{aligned}$$

$$s_1 = -200, \quad s_2 = -800$$

$$I_f = i_L(\infty) = 0.1 \text{ A} = 100 \text{ mA}$$

$$i_L(0) = I_f + A_1 + A_2 = 0.1$$

$$A_1 + A_2 = 0 \quad \text{--- (1)}$$

Name:

Solutions (7)

March 6, 2017

UTEP ID:

EE 2351 Test 1 Spring 2017

$$\frac{di_L(0^+)}{dt} = s_1 A_1 + s_2 A_2 = \frac{v_L(0^+)}{L} = \frac{v_C(0^+)}{L} = \frac{75}{250 \times 10^{-3}}$$

$$-200 A_1 - 800 A_2 = 300 \text{ A/s}$$

$$-2 A_1 - 8 A_2 = 3 \quad (2)$$

from (1)  $\Rightarrow A_1 = -A_2$

Substituting in (2)  $-2 A_1 + 8 A_1 = 3$

$$6 A_1 = 3$$

$$\begin{array}{l} A_1 = 0.5 \\ A_2 = -0.5 \end{array}$$

$$i_L(t) = 0.1 + 0.5 e^{-200t} - 0.5 e^{-800t} \text{ A for } t \geq 0$$