


Course Instructor
Dr. Raymond C. Rumpf
Office: A-337
Phone: (915) 747-6958
E-Mail: rcrumpf@utep.edu




EE 4347
Applied Electromagnetics

Topic 4e

Impedance Transformation and Parameter Relations


◆◆ These notes may contain copyrighted material obtained under fair use rules. Distribution of these materials is strictly prohibited ◆◆

Lecture Outline



- Input Impedance, Z_{in}
- Parameter Relations
- Special Cases of Terminated Transmission Lines
 - Shorted line ($Z_L = 0$)
 - Open-circuit line ($Z_L = \infty$)
 - Matched line ($Z_L = Z_0$)

Impedance Transformation & Parameters



Slide 2

Input Impedance, Z_{in}

Impedance Transformation & Parameters

Slide 3

Problem Setup APPLIED EM

The diagram illustrates the setup for calculating input impedance. A generator with voltage V_g and internal impedance Z_g is connected to a transmission line of length l . The transmission line has characteristic impedance Z_0 and propagation constant γ . A load impedance Z_L is connected at the end of the line. The input impedance Z_{in} is defined at the generator end. A coordinate z is shown along the line, with $z = -l$ at the generator end and $z = 0$ at the load end.

The simplified circuit shows the generator and its internal impedance Z_g connected to the input impedance Z_{in} at the generator end. The coordinate $z = -l$ is indicated.

The input impedance Z_{in} is the impedance observed by the generator.

The input impedance Z_{in} is NOT necessarily the line's characteristic impedance Z_0 or the load impedance Z_L .

Impedance Transformation & Parameters Slide 4

Animation of Impedance Transformation

APPLIED EM

$L = 0.00\lambda$
 $Z_{in}(0) = 10.00 + j10.00 \Omega$
 $Z_L = 10.00 + j10.00 \Omega$

$$Z_{in}\left(\frac{\lambda}{4} + m\frac{\lambda}{2}\right) = \frac{Z_0^2}{Z_L}$$

Input impedance inverts

$$Z_{in} = 125 - j125 \Omega$$

$$Z_{in}\left(m\frac{\lambda}{2}\right) = Z_L$$

Input impedance repeats

$$Z_{in} = 10 + j10 \Omega$$

Impedance Transformation & Parameters
Slide 5

Derivation of Input Impedance, Z_{in} (1 of 2)

APPLIED EM

The reflection coefficient at any point z from the load is

$$\Gamma(z) = \frac{\overset{\text{Backward Wave}}{V_0^- e^{\gamma z}}}{\underset{\text{Forward Wave}}{V_0^+ e^{-\gamma z}}} = \frac{V_0^-}{V_0^+} e^{2\gamma z}$$

This means that from the perspective of the generator, the reflection going into the transmission line will change depending on the length of the transmission line. This can only happen if the input impedance to the transmission line is changing.

Impedance Transformation & Parameters
Slide 6

Derivation of Input Impedance, Z_{in} (2 of 2)



We define the impedance of the line at position z to be

$$Z(z) = \frac{V(z)}{I(z)}$$

We previously wrote $V(z)$ and $I(z)$ as

$$V(z) = V_0^+ (e^{-\gamma z} + \Gamma_L e^{\gamma z})$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-\gamma z} - \Gamma_L e^{\gamma z})$$

$$\Gamma_L = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Substituting in our expressions for $V(z)$ and $I(z)$ gives

$$Z(z) = \frac{\cancel{V_0^+} (e^{-\gamma z} + \Gamma_L e^{\gamma z})}{\cancel{V_0^+} / Z_0 (e^{-\gamma z} - \Gamma_L e^{\gamma z})} = Z_0 \frac{e^{-\gamma z} + \Gamma_L e^{\gamma z}}{e^{-\gamma z} - \Gamma_L e^{\gamma z}}$$

It makes sense that the impedance is not a function of voltage in a linear system.

Impedance Transformation & Parameters



Slide 7

Sanity Check: Input Impedance at Load



The input impedance at the load can be determined by setting $z = 0$ in our previous equation.

$$Z_{in}(0) = Z_0 \frac{\cancel{V_0^+} + \Gamma_L \cancel{V_0^+}}{\cancel{V_0^+} - \Gamma_L \cancel{V_0^+}}$$

$$e^{-\gamma \cdot 0} = 1$$

$$= Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

Cancel e^0 from the equation.

$$= Z_0 \frac{1 + \frac{Z_L - Z_0}{Z_L + Z_0}}{1 - \frac{Z_L - Z_0}{Z_L + Z_0}}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= Z_0 \frac{Z_L + \cancel{Z_0} + Z_L - \cancel{Z_0}}{\cancel{Z_0} + Z_0 - \cancel{Z_0} + Z_0}$$

Multiply numerator and denominator by $Z_L + Z_0$.

$$= Z_0 \frac{2Z_L}{2Z_0}$$

Cancel Z_0 in numerator and Z_L in denominator.

$$= Z_L$$

We got the answer we were expecting!

Impedance Transformation & Parameters



Slide 8

Input Impedance at $z = -\ell$



The input impedance at location $z = -\ell$ is

$$Z_{\text{in}}(-\ell) = Z_0 \frac{e^{-\gamma(-\ell)} + \Gamma_L e^{\gamma(-\ell)}}{e^{-\gamma(-\ell)} - \Gamma_L e^{\gamma(-\ell)}} = Z_0 \frac{e^{\gamma\ell} + \Gamma_L e^{-\gamma\ell}}{e^{\gamma\ell} - \Gamma_L e^{-\gamma\ell}}$$

A Note About Sign: Backing away from the load, z becomes negative. However, we defined $z = -\ell$ so ℓ stays positive in this equation and for equations that follow.

Impedance Transformation & Parameters



Slide 9

Impedance Transformation Formula (1 of 2)



Recall that

$$Z(-\ell) = Z_0 \frac{e^{\gamma\ell} + \Gamma_L e^{-\gamma\ell}}{e^{\gamma\ell} - \Gamma_L e^{-\gamma\ell}} \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

We can eliminate Γ_L from the input impedance equation by substituting in our expression for Γ_L .

$$Z_{\text{in}}(-\ell) = Z_0 \frac{e^{\gamma\ell} + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-\gamma\ell}}{e^{\gamma\ell} - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-\gamma\ell}} = Z_0 \frac{Z_L (e^{\gamma\ell} + e^{-\gamma\ell}) + Z_0 (e^{\gamma\ell} - e^{-\gamma\ell})}{Z_L (e^{\gamma\ell} - e^{-\gamma\ell}) + Z_0 (e^{\gamma\ell} + e^{-\gamma\ell})}$$

$\cosh(z) = \frac{e^z + e^{-z}}{2}$ $\sinh(z) = \frac{e^z - e^{-z}}{2}$

$$= Z_0 \frac{Z_L \cdot 2 \cosh(\gamma\ell) + Z_0 \cdot 2 \sinh(\gamma\ell)}{Z_L \cdot 2 \sinh(\gamma\ell) + Z_0 \cdot 2 \cosh(\gamma\ell)}$$

Impedance Transformation & Parameters



Slide 10

Impedance Transformation Formula (2 of 2)



Recall that

$$\tanh(z) = \frac{\sinh(z)}{\cosh(z)}$$

This lets us write the input impedance expression as

$$Z_{\text{in}}(-\ell) = Z_0 \frac{Z_L \cdot 2 \cosh(\gamma\ell) + Z_0 \cdot 2 \sinh(\gamma\ell)}{Z_L \cdot 2 \sinh(\gamma\ell) + Z_0 \cdot 2 \cosh(\gamma\ell)} = Z_0 \frac{Z_L + Z_0 \frac{\sinh(\gamma\ell)}{\cosh(\gamma\ell)}}{Z_L \frac{\sinh(\gamma\ell)}{\cosh(\gamma\ell)} + Z_0}$$

$$Z_{\text{in}}(-\ell) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma\ell)}{Z_0 + Z_L \tanh(\gamma\ell)}$$

Impedance Transformation & Parameters



Slide 11

Input Transformation for Lossless Line



The lossless line has

$$\alpha = 0$$

$$\gamma = j\beta$$

Putting these values into our impedance transformation formula gives

$$Z_{\text{in}}(-\ell) = Z_0 \frac{Z_L + Z_0 \tanh(j\beta\ell)}{Z_0 + Z_L \tanh(j\beta\ell)}$$

Recognizing that $\tanh(jz) = j\tan(z)$, the expression for lossless lines becomes

$$Z_{\text{in}}(-\ell) = Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)}$$

Impedance Transformation & Parameters



Slide 12

Input Impedance Repeats for Lossless Lines



For lossless lines, the $\tan(\beta\ell)$ function in the impedance transformation equation tells us that the function is periodic and repeats.

The function repeats every integer multiple of π .

$$\beta\ell \pm m\pi \quad m = -\infty, \dots, -3, -2, -1, 0, 1, 2, 3, \dots, \infty$$

Recognizing that $\beta = 2\pi/\lambda$, the above expression leads to

$$\ell \pm m \frac{\lambda}{2} \quad \text{Note: } \lambda \text{ is the wavelength in the transmission line, not the free space wavelength } \lambda_0.$$

This means the input impedance repeats for every half-wavelength long the transmission line is.

We will revisit this when we cover Smith charts, which will give you a way to visualize the impedance transformation phenomenon.

Impedance Transformation & Parameters




Slide 13

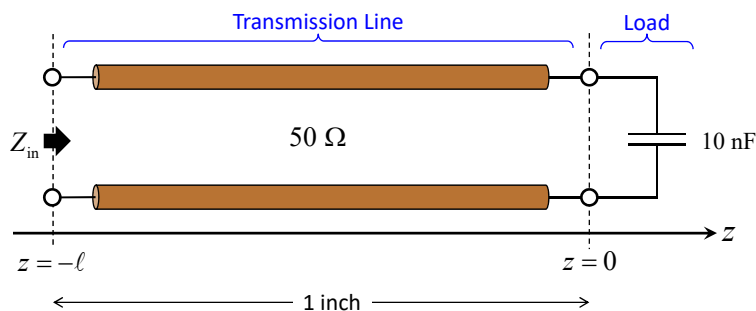Example: Impedance Transformation (1 of 3)



A transmission line with 50Ω characteristic impedance is connected to a 10 nF capacitor as the load. If the phase constant of the transmission line is $\beta = 60 \text{ m}^{-1}$, what is the input impedance Z_{in} of a 1 inch section of line operating at 4.0 GHz ? What equivalent circuit would the source see?



Impedance Transformation & Parameters



Slide 14

Example: Impedance Transformation (2 of 3)



Loss was not specified so we assume a lossless transmission line. Our impedance transformation equation is therefore

$$Z_{\text{in}}(-\ell) = Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)}$$

The variables in this equation are

$$Z_0 = 50 \Omega$$

$$\beta\ell = (60 \text{ m}^{-1})(1 \text{ inch}) \left(\frac{2.54 \text{ cm}}{1 \text{ inch}} \right) \left(\frac{1 \text{ m}}{100 \text{ cm}} \right) = 1.524$$

$$Z_L = \frac{1}{j\omega C} = \frac{1}{j2\pi fC} = \frac{1}{j2\pi(4.0 \times 10^9 \text{ s}^{-1})(10 \times 10^{-9} \text{ F})} = -j0.004 \Omega$$

Impedance Transformation & Parameters



Slide 15

Example: Impedance Transformation (3 of 3)



Substituting these values into the impedance transformation equation gives

$$Z_{\text{in}} = (50 \Omega) \left[\frac{(-j0.004 \Omega) + j(50 \Omega) \tan(60 \cdot 0.0254)}{(50 \Omega) + j(-j0.004 \Omega) \tan(60 \cdot 0.0254)} \right] = \boxed{j1.07 \times 10^3 \Omega}$$

The input impedance is purely imaginary and positive. Thus, the input impedance looks like an inductor to the generator.

$$Z_{\text{in}} = j\omega L_{\text{eq}}$$

$$L_{\text{eq}} = \frac{Z_{\text{in}}}{j\omega} = \frac{Z_{\text{in}}}{j2\pi f} = \frac{j1.07 \times 10^3 \Omega}{j2\pi(4.0 \times 10^9 \text{ s}^{-1})} = 4.24 \times 10^{-8} \text{ H} = \boxed{42.4 \text{ nH}}$$

Impedance Transformation & Parameters



Slide 16

Parameter Relations

Impedance Transformation & Parameters



Slide 17

V_{\max} , V_{\min} , I_{\max} & I_{\min} in Terms of VSWR



V_{\max} and V_{\min}

$$V_{\max} = |V_0^+| (1 + |\Gamma_L|) = |V_0^+| \frac{2 \text{VSWR}}{\text{VSWR} + 1}$$

$$V_{\min} = |V_0^+| (1 - |\Gamma_L|) = |V_0^+| \frac{2}{\text{VSWR} + 1}$$

I_{\max} and I_{\min}

$$I_{\max} = \frac{|V_0^+|}{Z_0} (1 + |\Gamma_L|) = \frac{|V_0^+|}{Z_0} \frac{2 \text{VSWR}}{\text{VSWR} + 1}$$

$$I_{\min} = \frac{|V_0^+|}{Z_0} (1 - |\Gamma_L|) = \frac{|V_0^+|}{Z_0} \frac{2}{\text{VSWR} + 1}$$

Impedance Transformation & Parameters



Slide 18

Z_0 in Terms of VSWR



The characteristic impedance Z_0 can be calculated from V_{\max} and I_{\max} or V_{\min} and I_{\min} .

$$Z_0 = \frac{V_{\max}}{I_{\max}} = \frac{V_{\min}}{I_{\min}}$$

The input impedance Z_{in} repeats as you back away from the load. We can calculate the maximum and minimum impedance as

$$\max[Z_{\text{in}}] = \frac{V_{\max}}{I_{\min}} = Z_0 \cdot \text{VSWR}$$

$$\min[Z_{\text{in}}] = \frac{V_{\min}}{I_{\max}} = \frac{Z_0}{\text{VSWR}}$$

$$\min[Z_{\text{in}}] \leq Z_{\text{in}} \leq \max[Z_{\text{in}}]$$

Impedance Transformation & Parameters



Slide 19

Example (1 of 3)



A 50Ω impedance transmission line is connected to an antenna with a 72Ω input impedance. A source provides an input signal of 24 V peak-to-peak.

What is the reflection coefficient at the antenna?

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(72 \Omega) - (50 \Omega)}{(72 \Omega) + (50 \Omega)} = \boxed{0.1803}$$

In this case, the antenna is the load.

What fraction of the input power is delivered to the antenna?

$$R = |\Gamma_L|^2 = |0.1803|^2 = 0.0325$$

$$T = 1 - R = 1 - 0.0325 = 0.9675 = \boxed{96.7\%}$$

Despite the mismatch, almost all power is still delivered to the antenna. This still does not mean the antenna will radiate!

What is the VSWR on the line feeding the antenna?

$$\text{VSWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + |0.1803|}{1 - |0.1803|} = \boxed{1.44}$$

$$\text{VSWR}_{\text{dB}} = 20 \log_{10}(\text{VSWR}) = 20 \log_{10}(1.44) = \boxed{3.17 \text{ dB}}$$

Impedance Transformation & Parameters



Slide 20

Example (2 of 3)



What is the minimum and maximum voltage on the line?

First, we need to convert voltage peak-to-peak V_{p-p} to voltage magnitude V_0 .

$$V_0^+ = \frac{V_{p-p}}{2} = \frac{24 \text{ V}}{2} = 12 \text{ V}$$

Now we are in a position to calculate V_{\min} and V_{\max} .

$$V_{\min} = |V_0^+|(1 - |\Gamma_L|) = 12 \text{ V}(1 - 0.1803) = 9.84 \text{ V}$$

$$V_{\max} = |V_0^+|(1 + |\Gamma_L|) = 12 \text{ V}(1 + 0.1803) = 14.16 \text{ V}$$

When we are utilizing high voltages, we want to be sure V_{\max} will not cause arcing or any other breakdown problems.

What is the minimum and maximum current on the line?

$$I_{\min} = \frac{V_{\min}}{Z_0} = \frac{9.84 \text{ V}}{50 \Omega} = 0.1967 \text{ A}$$

$$I_{\max} = \frac{V_{\max}}{Z_0} = \frac{14.16 \text{ V}}{50 \Omega} = 0.2833 \text{ A}$$

At high power, we want to be sure I_{\max} will not cause heating problems.

Impedance Transformation & Parameters



Slide 21

Example (3 of 3)



What is the total range of input impedances a source could see?

$$\min[Z_{in}] = \frac{V_{\min}}{I_{\max}} = \frac{9.84 \text{ V}}{0.2833 \text{ A}} = 34.72 \Omega$$

$$\max[Z_{in}] = \frac{V_{\max}}{I_{\min}} = \frac{14.16 \text{ V}}{0.1967 \text{ A}} = 72 \Omega$$

$$\min[Z_{in}] \leq Z_{in} \leq \max[Z_{in}]$$

$$34.72 \Omega \leq Z_{in} \leq 72 \Omega$$

Impedance Transformation & Parameters



Slide 22

Special Cases of Terminated Transmission Lines

Impedance Transformation & Parameters

Slide 23

Shorted Line, $Z_L = 0$



Reflection from Load

$$\Gamma_L = -1$$

V_{\min} and V_{\max}

$$V_{\min} = 0$$

$$V_{\max} = 2|V_0^+|$$

Input Impedance

$$Z_{\text{in}}(-\ell) = \begin{cases} Z_0 \tanh \gamma \ell & \text{lossy} \\ jZ_0 \tan \beta \ell & \text{lossless} \end{cases}$$

Note 1: Z_{in} for the lossless line is purely imaginary. This means it is purely reactive and no dissipation occurs in the line. The input impedance alternates between being capacitive and inductive as you back away from the load.

Voltage Standing Wave Ratio

$$\text{VSWR} = \infty \quad \text{There exists some } z \text{ where } V(z) = 0.$$

I_{\min} and I_{\max}

$$I_{\min} = 0$$

$$I_{\max} = \frac{2|V_0^+|}{Z_0}$$

$\min[Z_{\text{in}}]$ and $\max[Z_{\text{in}}]$

$$\min[Z_{\text{in}}] = 0 \quad \text{short circuit}$$

$$\max[Z_{\text{in}}] = \infty \quad \text{open circuit}$$

Note 2: The shorted line behaves much the same way as the open-circuit line. We also observe that

$$Z_{\text{in,short}} Z_{\text{in,open}} = Z_0^2$$

Impedance Transformation & Parameters

Slide 24

Open-Circuit Line, $Z_L = \infty$



Reflection from Load

$$\Gamma_L = +1$$

V_{\min} and V_{\max}

$$V_{\min} = 0$$

$$V_{\max} = 2|V_0^+|$$

Input Impedance

$$Z_{in}(-\ell) = \begin{cases} Z_0 \coth \gamma \ell & \text{lossy} \\ -jZ_0 \cot \beta \ell & \text{lossless} \end{cases}$$

Note 1: Z_{in} for the lossless line is purely imaginary. This means it is purely reactive and no dissipation occurs in the line. The input impedance alternates between being capacitive and inductive as you back away from the load.

Voltage Standing Wave Ratio

$$\text{VSWR} = \infty \quad \text{There exists some } z \text{ where } V(z) = 0.$$

I_{\min} and I_{\max}

$$I_{\min} = 0$$

$$I_{\max} = \frac{2|V_0^+|}{Z_0}$$

$\min[Z_{in}]$ and $\max[Z_{in}]$

$$\min[Z_{in}] = 0 \quad \text{short circuit}$$

$$\max[Z_{in}] = \infty \quad \text{open circuit}$$

Note 2: The open-circuit line behaves much the same way as the shorted line. We also observe that

$$Z_{in,short} Z_{in,open} = Z_0^2$$

Impedance Transformation & Parameters



Slide 25

Matched Line, $Z_L = Z_0$



Reflection from Load

$$\Gamma_L = 0$$

V_{\min} and V_{\max}

$$V_{\min} = V_{\max} = |V_0^+|$$

Input Impedance

$$Z_{in}(-\ell) = Z_0$$

Note: For the matched line, there are no reflections and all of the power is delivered to the load.

Voltage Standing Wave Ratio

$$\text{VSWR} = 1 \quad \text{because } V_{\max} = V_{\min}$$

I_{\min} and I_{\max}

$$I_{\min} = I_{\max} = |V_0^+|/Z_0$$

$\min[Z_{in}]$ and $\max[Z_{in}]$

$$\min[Z_{in}] = \max[Z_{in}] = Z_0$$

Impedance Transformation & Parameters



Slide 26