

Problem #1: Normalized Impedance and Admittance

Using just your calculator, answer the following questions:

- Given the characteristic impedance of a transmission line Z_0 , write the equations to calculate normalized impedance Z_L and normalized admittance Y_L .
 $z_L = ?$
 $y_L = ?$
- Next, write the equations to “denormalize” the impedance and admittance given Z_0 .
 $Z_L = ?$
 $Y_L = ?$
- If $Z_0 = 75 \Omega$, what is the normalized impedance given $Z_L = 25 + j100 \Omega$?
- If $Z_0 = 60 \Omega$, what is the impedance given the normalized impedance $z_L = 2 + j0.5$?
- If $Z_0 = 30 \Omega$, what is the normalized admittance given $Y_L = 0.1 + j0.02 \Omega^{-1}$?
- If $Z_0 = 55 \Omega$, what is the admittance given the normalized admittance $y_L = 2 + j1$?

Problem #2: Converting Between Impedance and Admittance

Given the characteristic impedance of a transmission line is 50Ω , calculate the following by hand and using the Smith chart. Include your Smith Charts showing your work with this assignment.

- Calculate Y_L given $Z_L = 150 - j25 \Omega$.
- Calculate Z_L given $Y_L = 0.3 - j0.1 \Omega^{-1}$.

Problem #3: Impedance Transformation

- A lossless transmission line has distributed parameters $C = 150 \text{ pF/m}$ and $L = 375 \text{ nH/m}$. It operates at 2.4 GHz and is connected to a load with impedance $15 - j25 \Omega$. Use a Smith chart to calculate the input impedance 2.0 cm from the load. Also determine the VSWR of the circuit.
- A lossless transmission line has distributed parameters $C = 100 \text{ pF/m}$ and $L = 250 \text{ nH/m}$. It operates at 1.0 GHz and is connected to a load with impedance $25 + j100 \Omega$. Use a Smith chart to calculate the input impedance 1.6 cm from the load. Also determine the VSWR of the circuit.

Note: Include your Smith Charts showing your work with this assignment.

Problem #4: Single Stub Tuning

A 75Ω transmission line operates at 5.0 GHz and is composed of two conductors suspended in air. The line feeds a load with complex impedance $Z_L = 75 - j30 \Omega$. Design a single stub tuning network to match the transmission line to the load. Draw a diagram of your design. What is the resulting VSWR after the matching circuit is incorporated? Provide your Smith Chart showing your work with this assignment.