




# TRANSMISSION LINES

EE 4347 Applied Electromagnetics

Pioneering 21<sup>st</sup> Century  
Electromagnetics and Photonics

<http://emlab.utep.edu/>

## Transmission Line Model

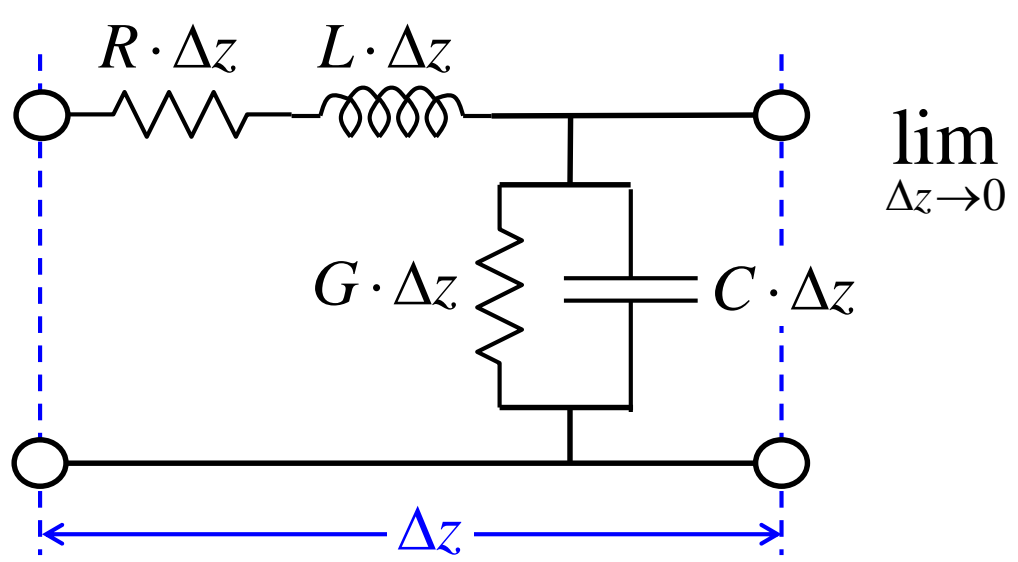

$R \equiv$  distributed resistance ( $\Omega/m$ )  
 $L \equiv$  distributed inductance (H/m)  
 $G \equiv$  distributed conductance ( $1/\Omega \cdot m$ )  
 $C \equiv$  distributed capacitance (F/m)

## Transmission Line Equations

$$-\frac{\partial V(z,t)}{\partial z} = R \cdot I(z,t) + L \frac{\partial I(z,t)}{\partial t}$$

$$-\frac{\partial I(z,t)}{\partial z} = G \cdot V(z,t) + C \frac{\partial V(z,t)}{\partial t}$$

## Transmission Line Wave Equations

$$\frac{d^2 V(z)}{dz^2} - (R + j\omega L)(G + j\omega C)V(z) = 0$$

$$\frac{d^2 I(z)}{dz^2} - (R + j\omega L)(G + j\omega C)I(z) = 0$$

## Solutions to TL Wave Equations

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

## Line Parameters

Characteristic Impedance

$$Z_0 = \frac{V_0^+}{I_0^+} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = R_0 + jX_0$$

Complex Propagation Constant

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\alpha = \sqrt{\frac{RG - \omega^2 LC + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}}{2}}$$

$$\beta = \sqrt{\frac{-RG + \omega^2 LC + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}}{2}}$$

Lossless Lines ( $R = G = 0$ )

$$\alpha = 0 \quad \beta = \omega \sqrt{LC}$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad R_0 = \sqrt{\frac{L}{C}} \quad X_0 = 0$$

Distortionless Lines ( $RC = LG$ )

$$\alpha = \sqrt{RG} \quad \beta = \omega \sqrt{LC}$$

$$Z_0 = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}} \quad R_0 = Z_0 \quad X_0 = 0$$

Misc.

$$Z_{in,short} Z_{in,open} = Z_0^2$$

$$P_{avg} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

## Impedance Transformation

General Case (with Loss)

$$Z_{in}(\ell) = Z_0 \left( \frac{Z_L + Z_0 \tanh \gamma \ell}{Z_0 + Z_L \tanh \gamma \ell} \right)$$

Lossless Case

$$Z_{in}(\ell) = Z_0 \left( \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell} \right)$$

## Transmission Line Behavior

General	Short	Open	Matched
$Z_L$	$Z_L = 0$	$Z_L = \infty$	$Z_L = Z_0$
$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$	$\Gamma_L = -1$	$\Gamma_L = 1$	$\Gamma_L = 0$
Lossy	Lossy	Lossy	Lossy
$Z_{in}(\ell) = Z_0 \left( \frac{Z_L + Z_0 \tanh \gamma \ell}{Z_0 + Z_L \tanh \gamma \ell} \right)$	$Z_{in} = Z_0 \tanh \gamma \ell$	$Z_{in} = Z_0 \coth \gamma \ell$	$Z_{in} = Z_0$
Lossless	Lossless	Lossless	Lossless
$Z_{in}(\ell) = Z_0 \left( \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell} \right)$	$Z_{in} = jZ_0 \tan \beta \ell$	$Z_{in} = -jZ_0 \cot \beta \ell$	$Z_{in} = Z_0$
$V_{max} =  V_0^+  (1 +  \Gamma )$	$V_{max} = 2 V_0^+ $	$V_{max} = 2 V_0^+ $	$V_{max} =  V_0^+ $
$V_{min} =  V_0^+  (1 -  \Gamma )$	$V_{min} = 0$	$V_{min} = 0$	$V_{min} =  V_0^+ $
$I_{max} = ( V_0^+ /Z_0)(1 +  \Gamma )$	$I_{max} = 2 V_0^+ /Z_0$	$I_{max} = 2 V_0^+ /Z_0$	$I_{max} =  V_0^+ /Z_0$
$I_{min} = ( V_0^+ /Z_0)(1 -  \Gamma )$	$I_{min} = 0$	$I_{min} = 0$	$I_{min} =  V_0^+ /Z_0$
$VSWR = \frac{1 +  \Gamma }{1 -  \Gamma }$	$VSWR = \infty$	$VSWR = \infty$	$VSWR = 1$
$\max[Z_{in}] = Z_0 \cdot VSWR$	$\max[Z_{in}] = \infty$	$\max[Z_{in}] = \infty$	$\max[Z_{in}] = Z_0$
$\min[Z_{in}] = Z_0 / VSWR$	$\min[Z_{in}] = 0$	$\min[Z_{in}] = 0$	$\min[Z_{in}] = Z_0$

## Types of Transmission Lines

